

KATHMANDU UNIVERSITY
End Semester Examination
June/July, 2023

Marks Scored:

Level : B.E.

Year : II

Exam Roll No.:

Time: 30 mins.

Registration No.:

Course : EEEG 204
Semester : I

F. M. : 10

Date : 19 JUL 2023

SECTION "A"

[20Q. \times 0.5 = 10 marks]

Encircle the most appropriate option. Symbols have their usual meaning.

- Which of the following is true for N-type semiconductor?
 - Pentavalent impurities are added
 - Majority charge carriers are holes
 - Fermi Level is near valence band
 - Ratio of minority and majority charge carriers is unity
- The application of external voltage to the terminals of diode is termed as _____.
 - Scattering
 - Photon
 - Bias
 - Diffusion
- The reverse breakdown voltage of a diode refers to:
 - The voltage at which the diode conducts current in the reverse direction
 - The voltage at which the diode blocks current in the reverse direction
 - The maximum voltage that can be applied across the diode in the reverse direction without causing damage
 - The voltage at which the diode switches from forward bias to reverse bias
- How does a Zener diode regulate voltage?
 - By dissipating excess voltage as heat
 - By limiting the current flow in the circuit
 - By maintaining a constant voltage drop across its terminals
 - By converting AC voltage to DC voltage
- Find the output voltage V_A for the circuit shown in Figure 1
 - 12.6V
 - 13V
 - 19.3V
 - 19.7V
- In a center-tapped full wave rectifier, how many diodes are used?
 - 1
 - 2
 - 3
 - 4
- What is the voltage gain of a common base amplifier?
 - Less than 1
 - Equal to 1
 - Greater than 1
 - Depends on biasing condition
- In a common emitter configuration, the input current is:
 - Base current (I_B)
 - Emitter current (I_E)
 - Collector current (I_C)
 - Both base and emitter currents combined ($I_B + I_E$)

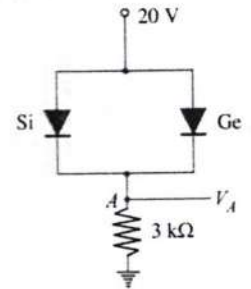


Figure 1

9. In CE configuration, BJT allows for amplification in _____.
 - a. Saturation region
 - b. Cut-off region
 - c. Active region
 - d. Reverse-biased region
10. Ideally, the input impedance of an op-amp is _____.
 - a. Very low
 - b. Very high
 - c. Equal to the output impedance
 - d. Zero
11. The summing amplifier configuration is often used in applications such as:
 - a. Audio amplification
 - b. Voltage regulation
 - c. Frequency modulation
 - d. Switching
12. Which of the following applications of op-amp does not require feedback?
 - a. Comparator
 - b. Integrator
 - c. Subtractor
 - d. Adder
13. Which logic gate gives an output of high (1) only if exactly one of its inputs is high (1)?
 - a. AND
 - b. OR
 - c. NOT
 - d. XOR
14. Which of the following is universal gate?
 - a. AND
 - b. OR
 - c. XOR
 - d. NAND
15. The Boolean expression $\bar{A}.B + A.\bar{B} + A.B$ is equivalent to
 - a. $A+B$
 - b. $\bar{A}.B$
 - c. $\bar{B}.+A$
 - d. $A.B$
16. Which Boolean identity states that performing the OR operation with the same variable will yield the same result as performing it once?
 - a. Idempotent Law
 - b. Identity Law
 - c. Distributive Law
 - d. Absorption Law
17. Which type of instrument works on the principle of attraction and repulsion?
 - a. PMMC
 - b. Moving Iron
 - c. Electrodynamicometer
 - d. Moving Coil
18. In moving iron instrument, the deflecting torque is proportional to:
 - a. Square of the current flowing through the moving coil
 - b. Current flowing through the moving coil
 - c. Magnetic field strength
 - d. Square of the magnetic field strength
19. Which type of instrument is most commonly used as a wattmeter?
 - a. PMMC instrument
 - b. Moving iron instrument
 - c. Electrodynamicometer instrument
 - d. None of the above
20. What is the purpose of signal conditioning in a data acquisition system?
 - a. To convert analog signals to digital format
 - b. To amplify and filter weak analog signals
 - c. To store and process digital data
 - d. To transmit data over a network

KATHMANDU UNIVERSITY
End Semester Examination
June/July, 2023

Level : B.E.
Year : II
Time : 2 hrs. 30 mins.

Course : EEG 204
Semester : I
F.M. : 40

SECTION "B"
[4Q × 10 = 40 marks]

19 JUL 2023

Attempt *ANY FOUR* questions. Missing data may be suitably assumed. Each symbol carries their usual meaning

1. a. Discuss the working of practical diodes with the help of V-I characteristic curve. [4]
b. Why is Zener Diode used as a voltage regulator? Explain. [3]
c. An a.c. supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10 : 1. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal [3]

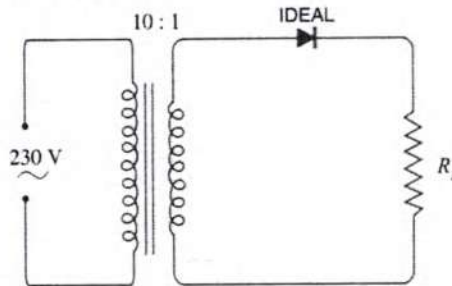


Figure 1

2. a. Derive the voltage gain for inverting and non-inverting op-amp. [3+3]
b. Design a subtractor using summing amplifiers and explain how it works. [4]
3. a. Explain the working principle of PNP transistor. [3]
b. In a common base connection, $\alpha = 0.95$. The voltage drop across 2 k Ω resistance which is connected in the collector is 2V. Find the base current. [3]

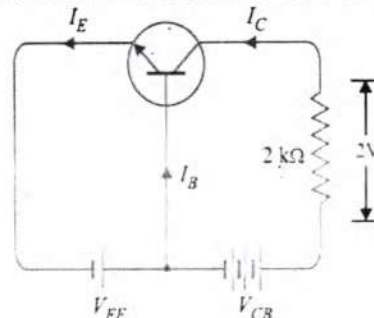


Figure 1

- c. Determine the Q point of the transistor circuit shown in Figure 3. Also draw the d.c. load line. Given $\beta = 200$ and $V_{BE} = 0.7V$ [4]

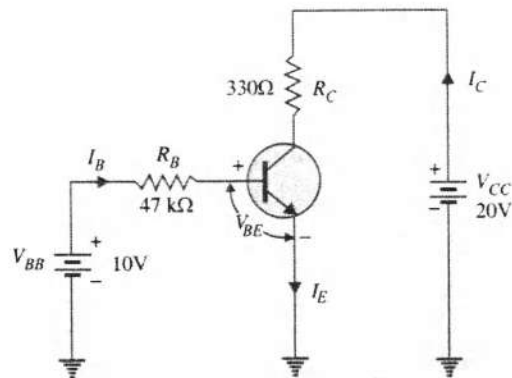


Figure 3

4. a. Construct XNOR gates using NOR gates only. Explain each step and mention all Boolean identities used. [4]
- b. Simplify: $F = \bar{A}\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}C + ABC$. Also, draw the logic diagram. [2+2]
- c. State duality principle. Write dual of function: $A.(B.C) = (A.B).C$ [2]
5. a. Explain the construction, working and torque equation of PMMC type instrument. [6]
- b. Explain Data Logger with its components. [4]